

4. Elemental 2-ports and Operational Amplifier

Ivan Maio

maio@polito.it

www.emc.polito.it





Part 4: Elemental 2-port ...

- 1. Controlled sources**
- 2. Nodal Analysis revisited**
- 3. Analysis of networks with controlled sources**
- 4. 2-port Elements**
- 5. Important 2-port elements**
 - 5.1. controlled sources
 - 5.2. ideal transformer
 - 5.3. operational amplifier

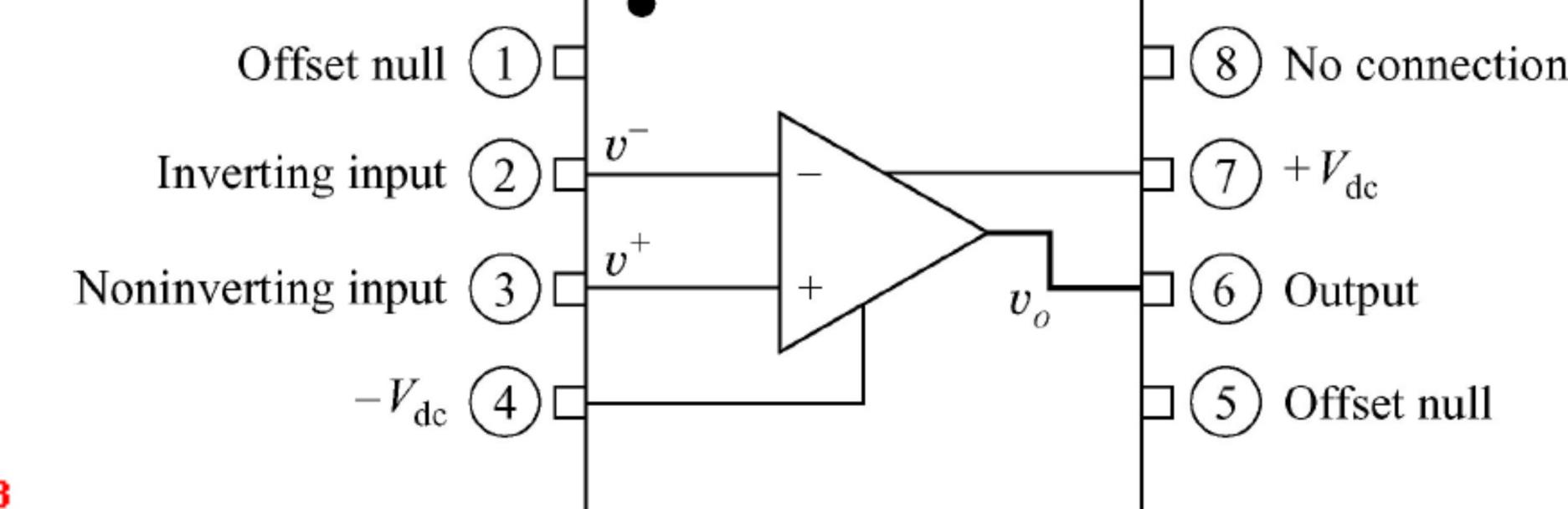
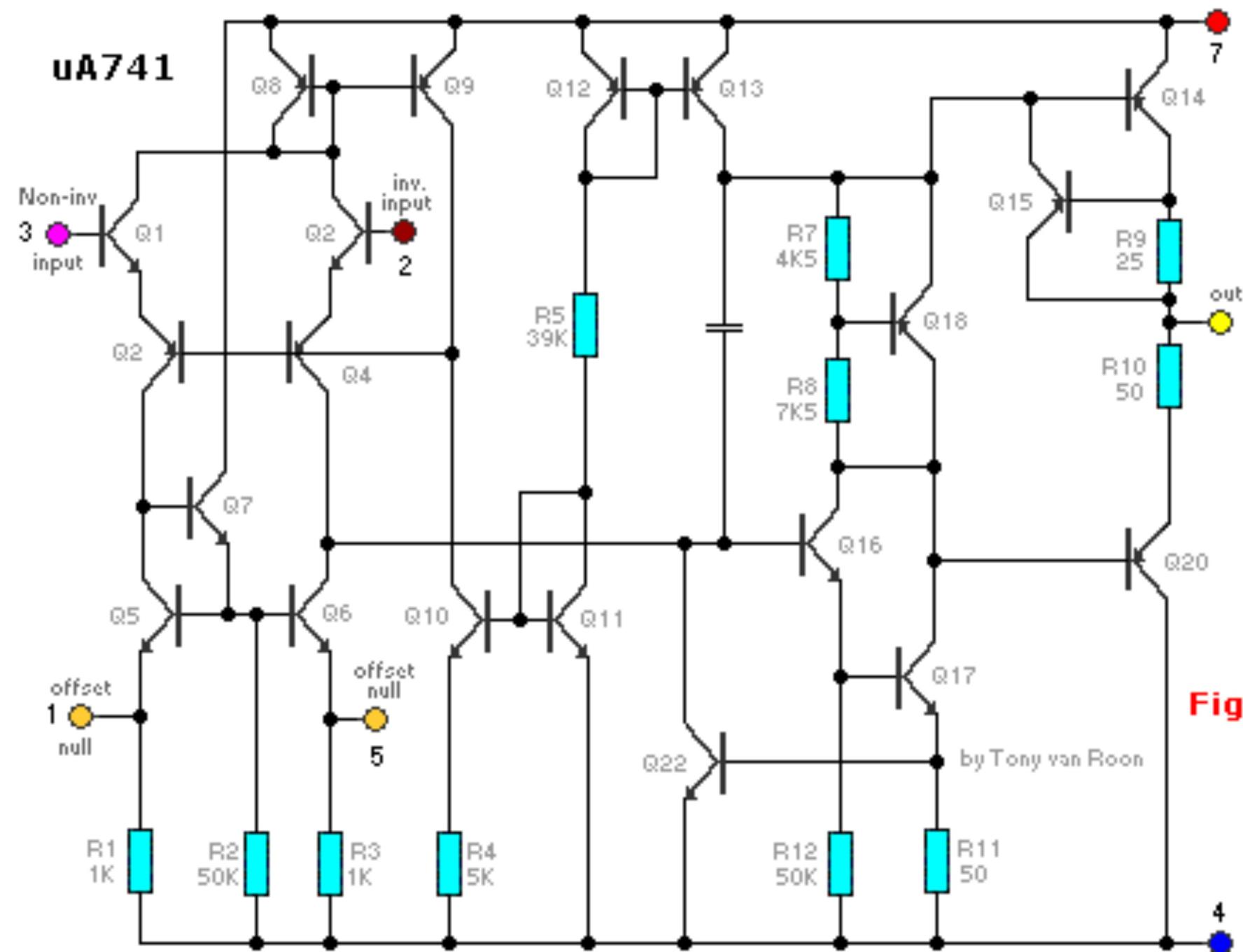
5. Important 2-port Elements: Operational Amplifier

multi-transistor 2-port amplifier with high voltage gain



5. Important 2-port Elements: Operational Amplifier

static models

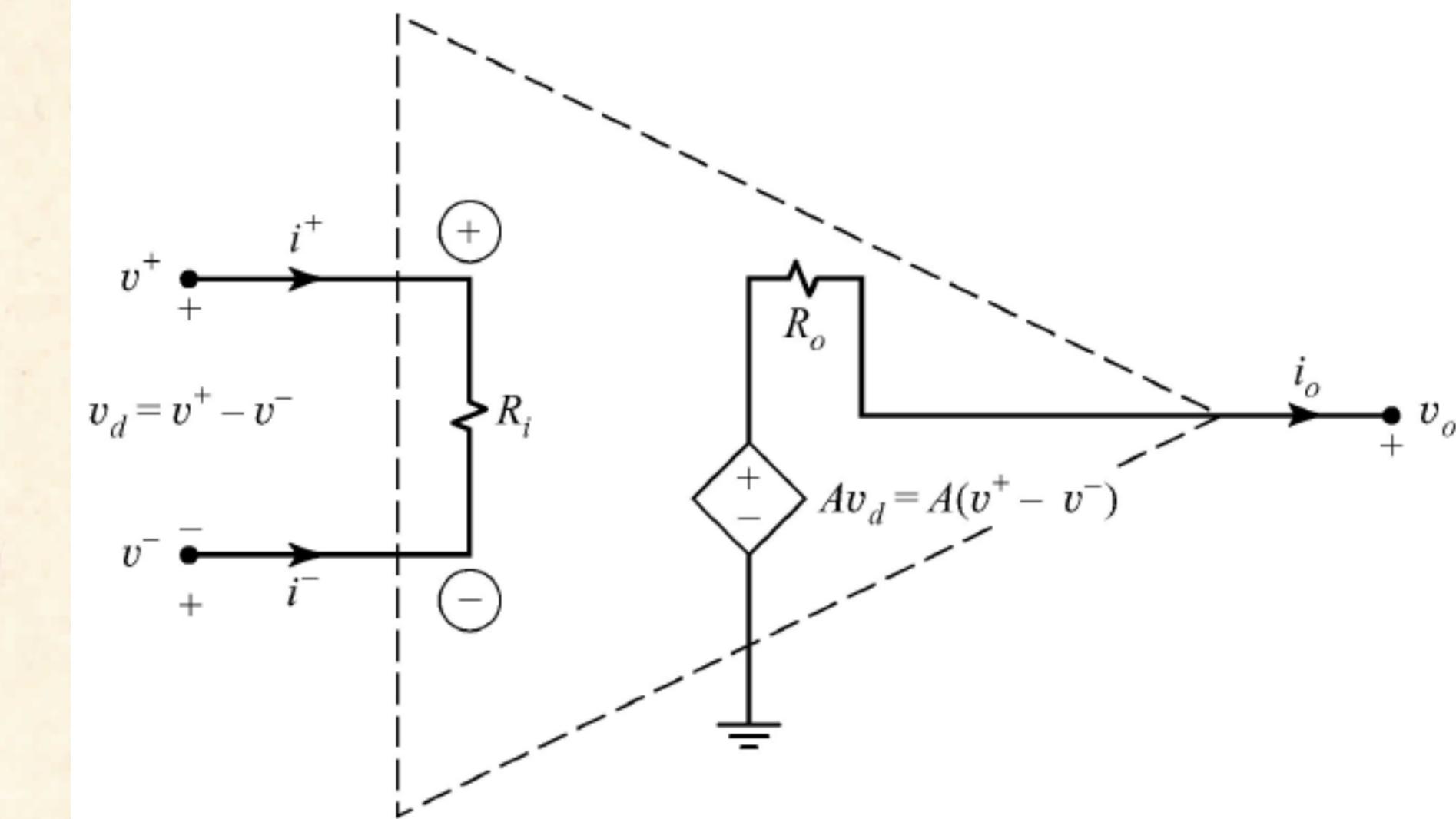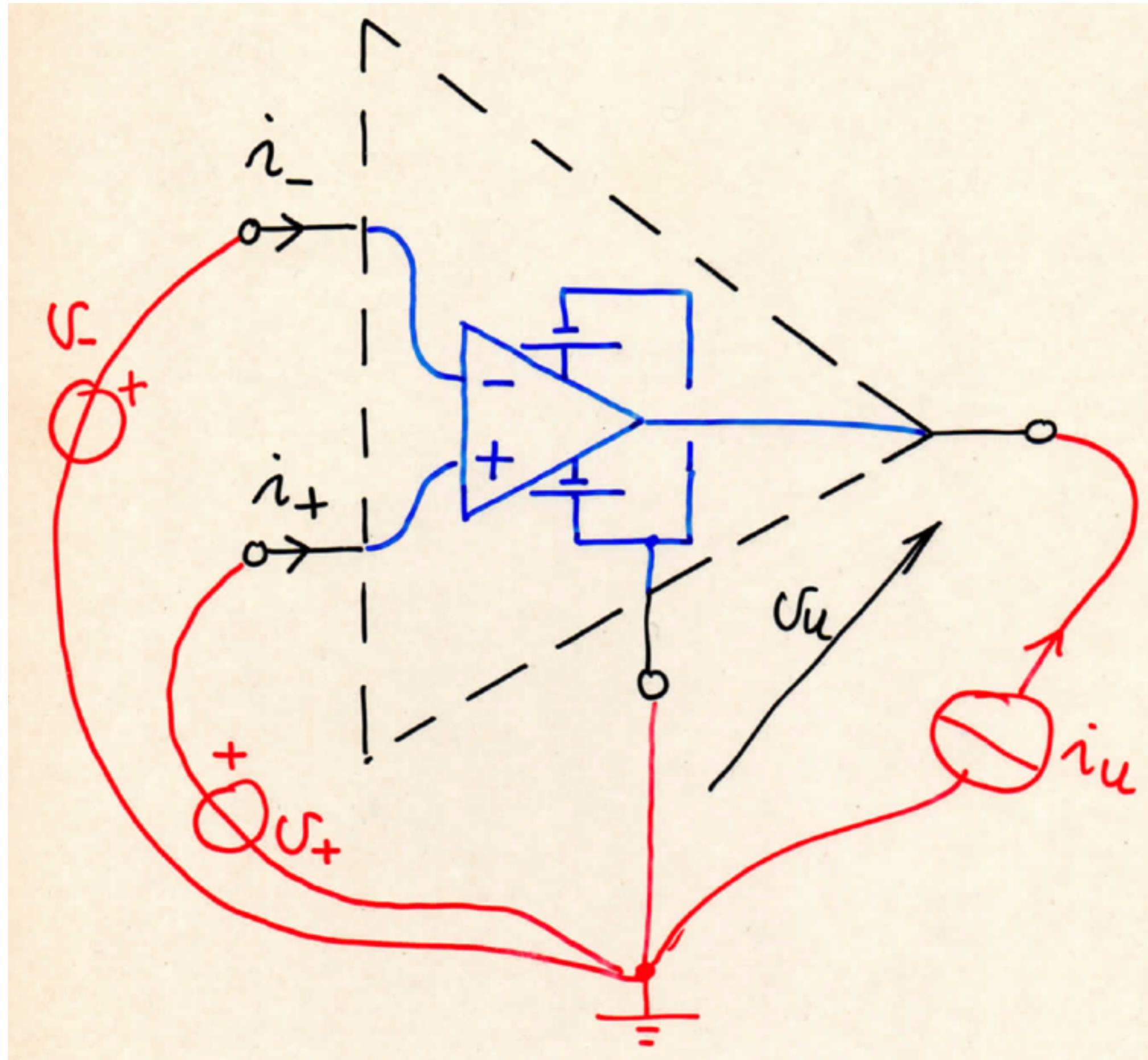


$$R_i \approx 10 \text{ k}\Omega$$

$$R_o \approx 10 \Omega$$

$$A \approx 10^5$$

5. Important 2-port Elements: Operational Amplifier


static models

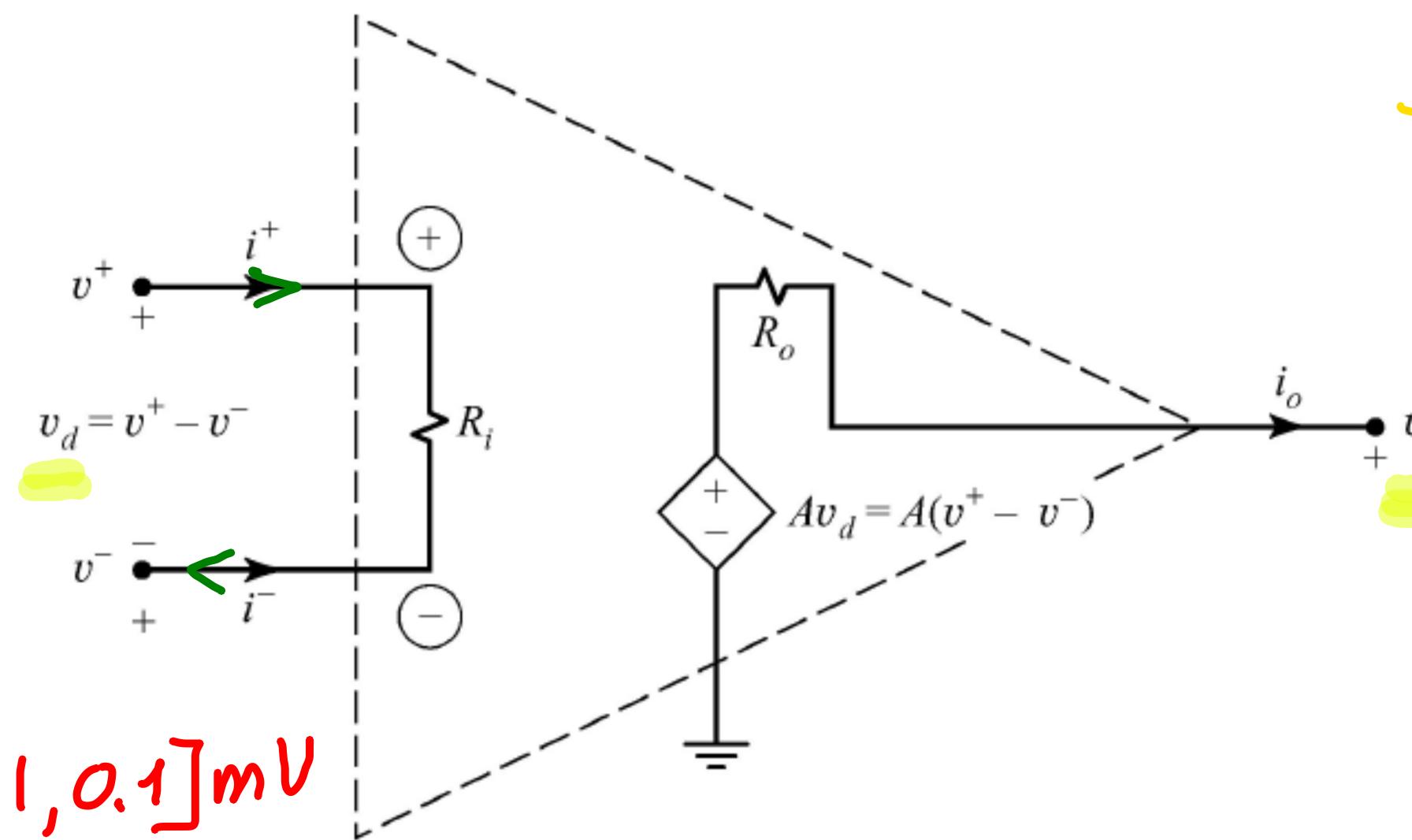

$$v_d \in [-0.1, 0.1] \text{ mV}$$

$$i^+ = -i^-$$

$$[-10, 10] \text{ nA}$$

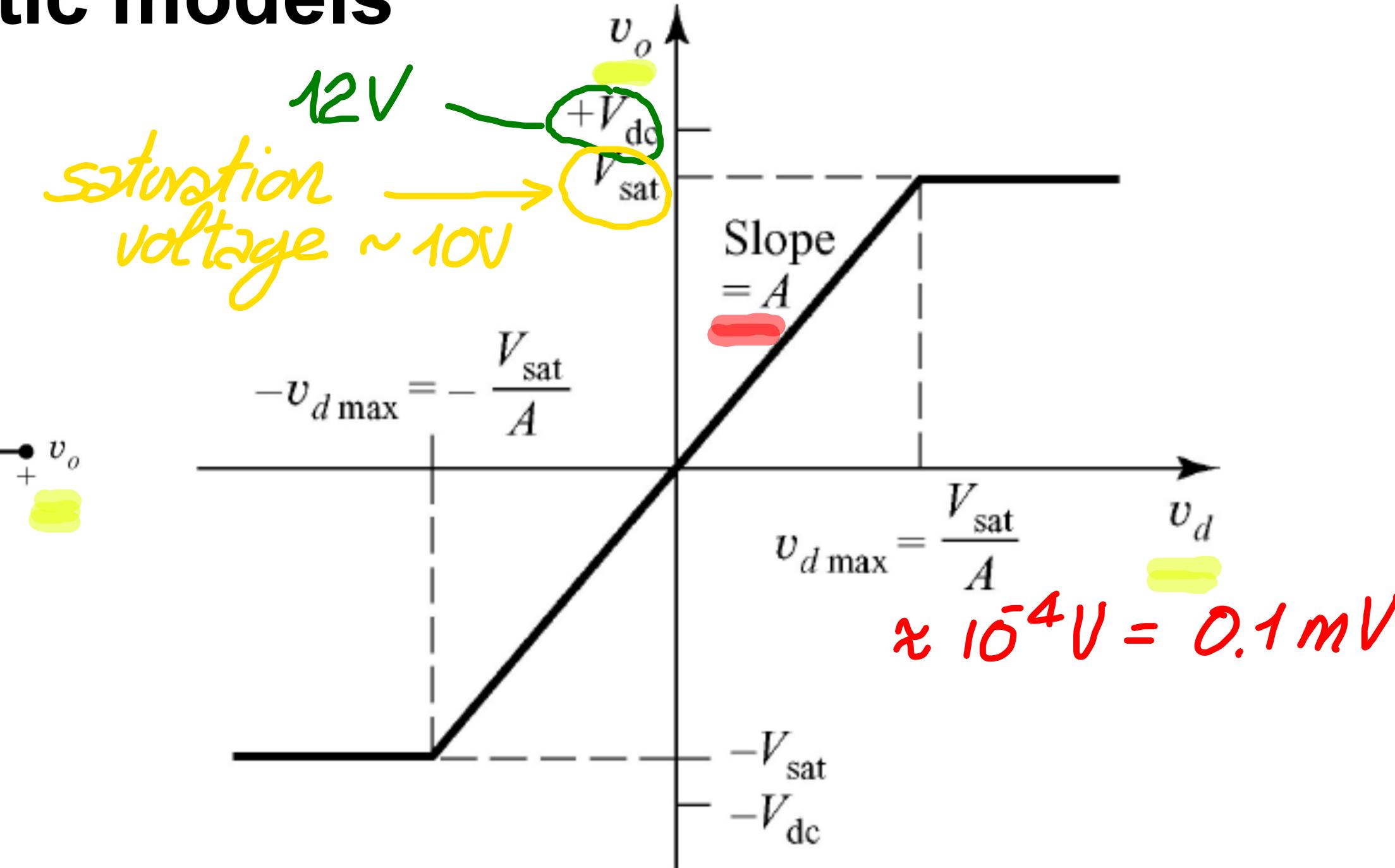

in linear region: v_d negligible $\rightarrow i^+$ and i^- negligible

5. The Ideal Operational Amplifier

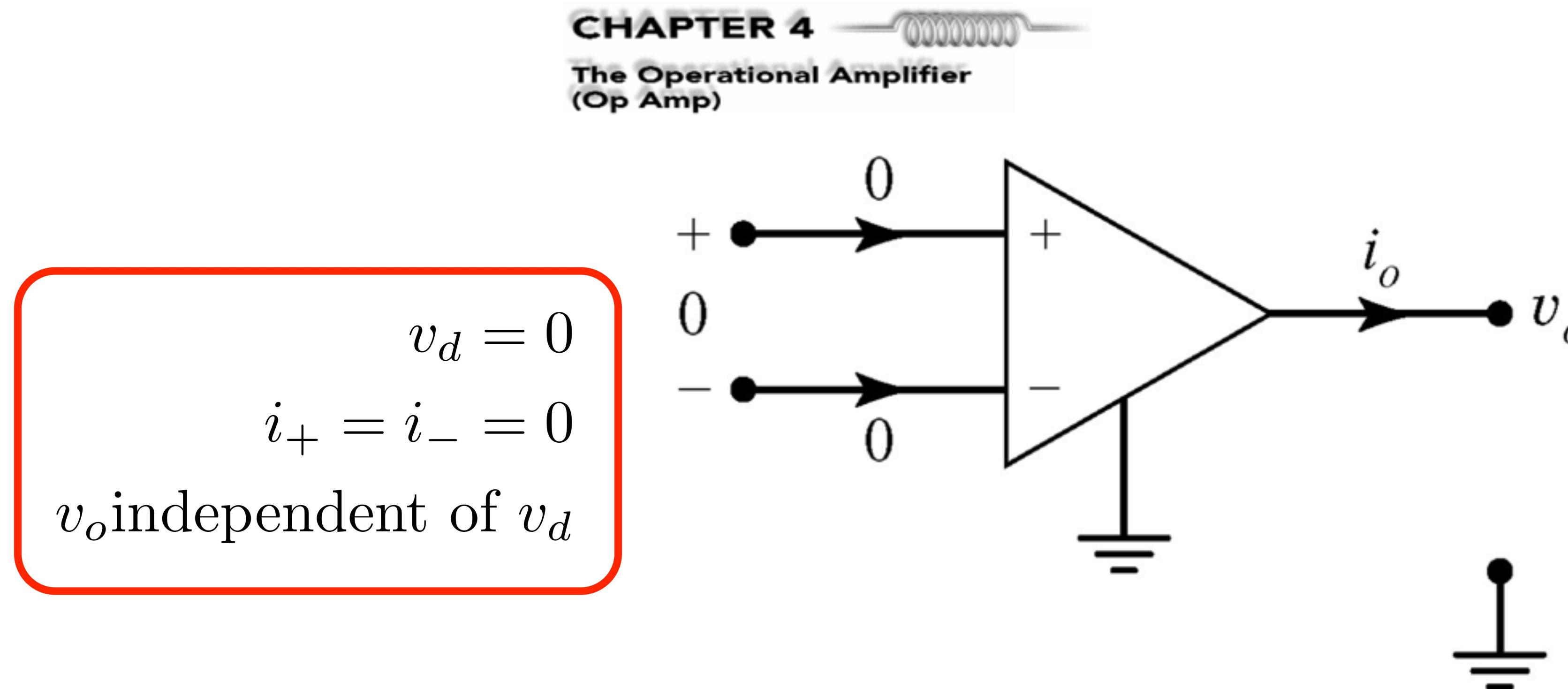



Figure 4.4
The ideal op amp and its virtual short-circuit properties.

Fundamentals of Electric Circuit Analysis, by Clayton Paul


5. The Ideal Operational Amplifier

Nullator, Norator and Nullor ...

Nullator

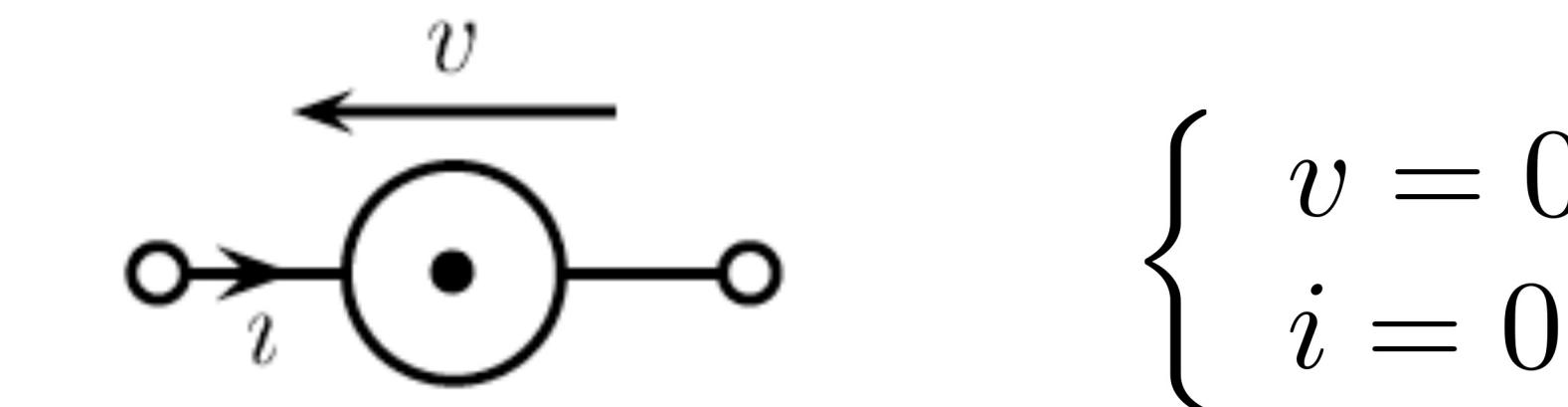

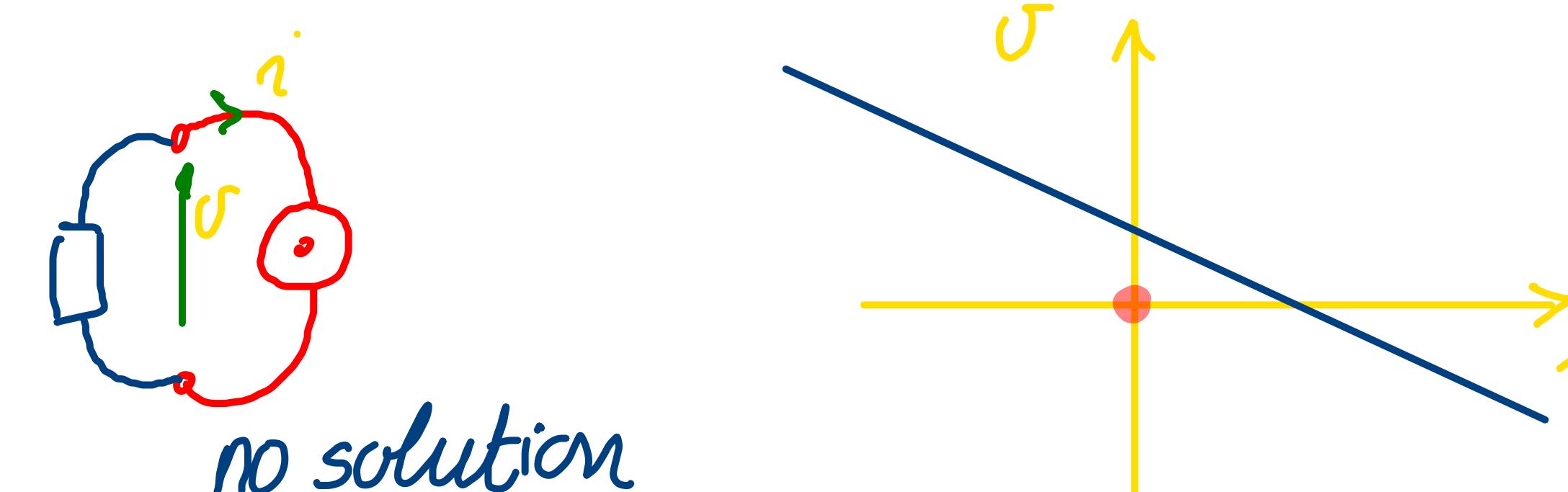
Resistive, linear, t-invariant, **over-constrained**



5. The Ideal Operational Amplifier



Nullator, Norator and Nullor ...

Norator

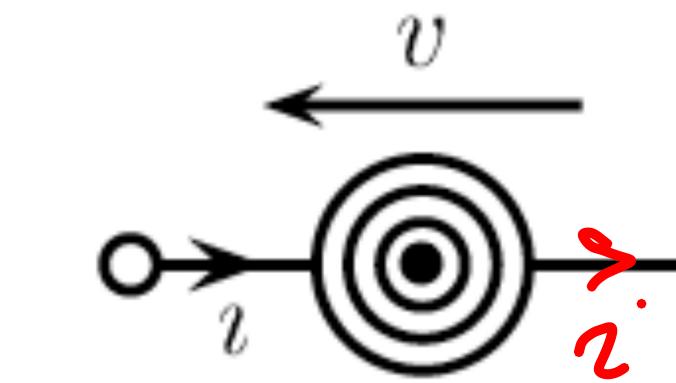

no constraints on
 v and i





under-constrained

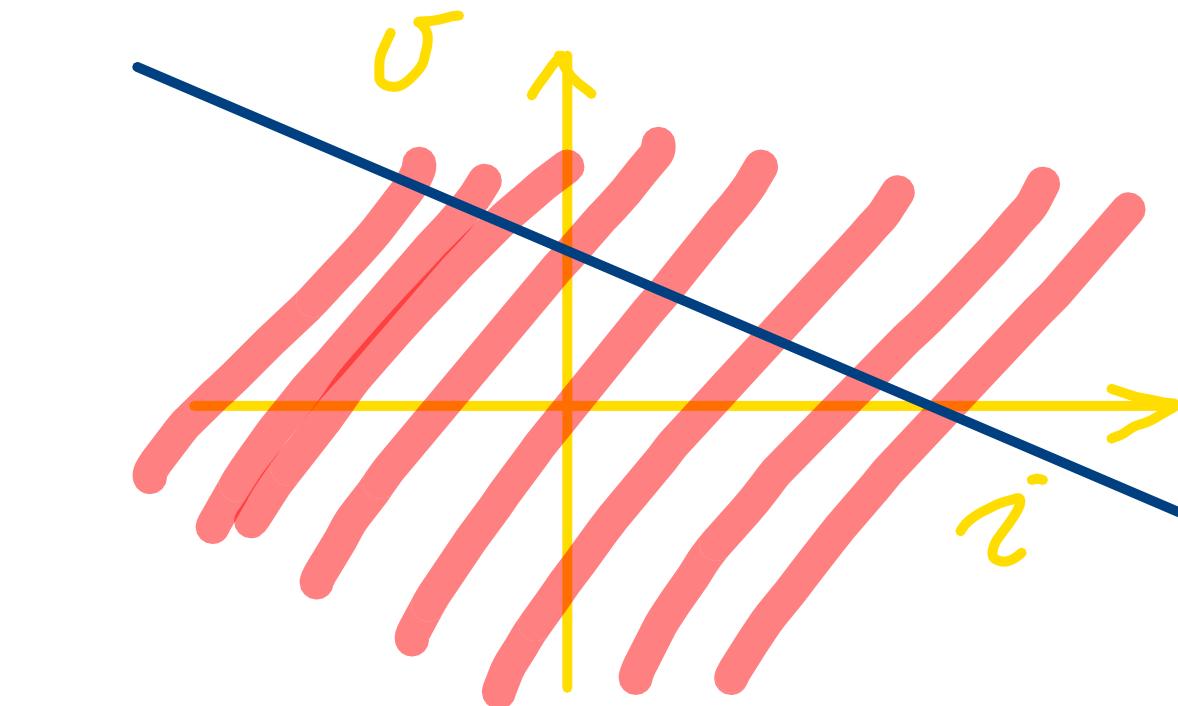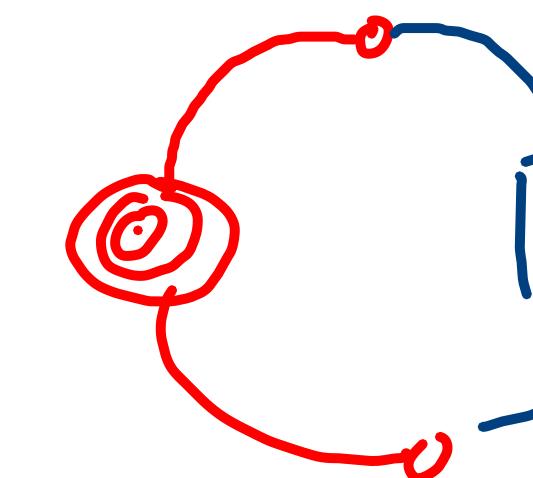

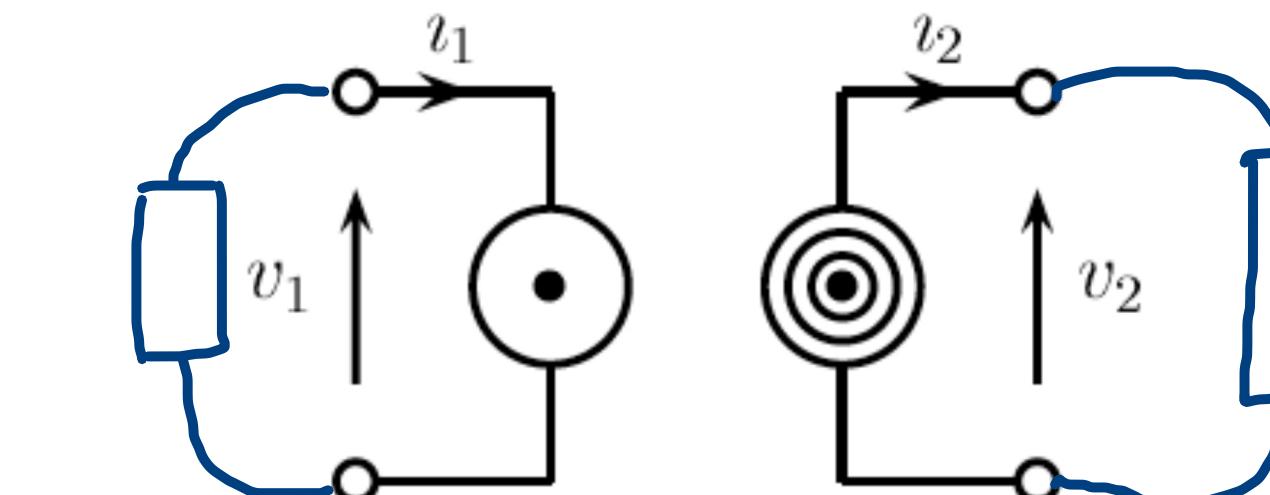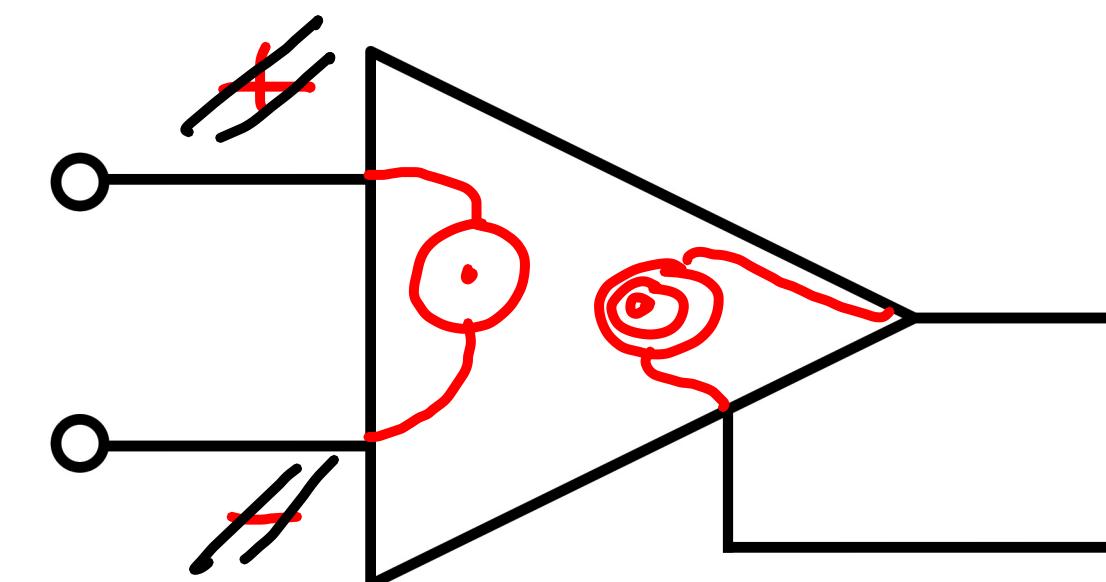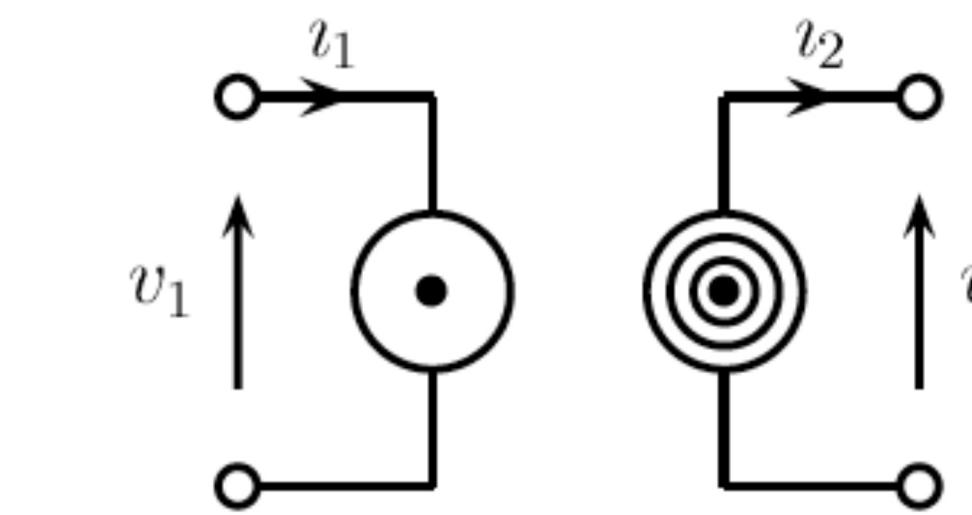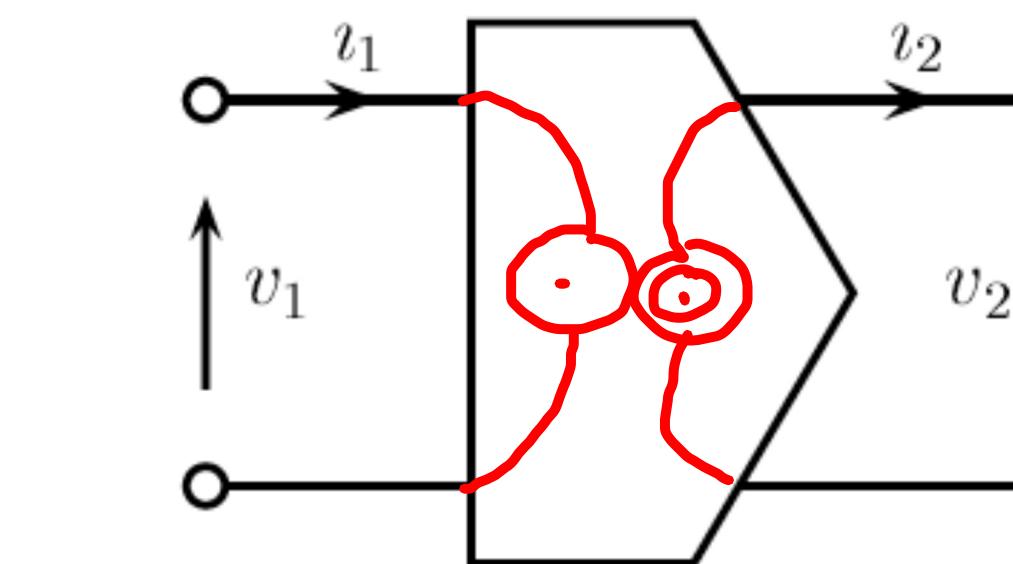5. The Ideal Operational Amplifier

Nullor or Ideal Operational Amplifier (OA)


intrinsic 2-port composed of one nullator and one norator



still no solution

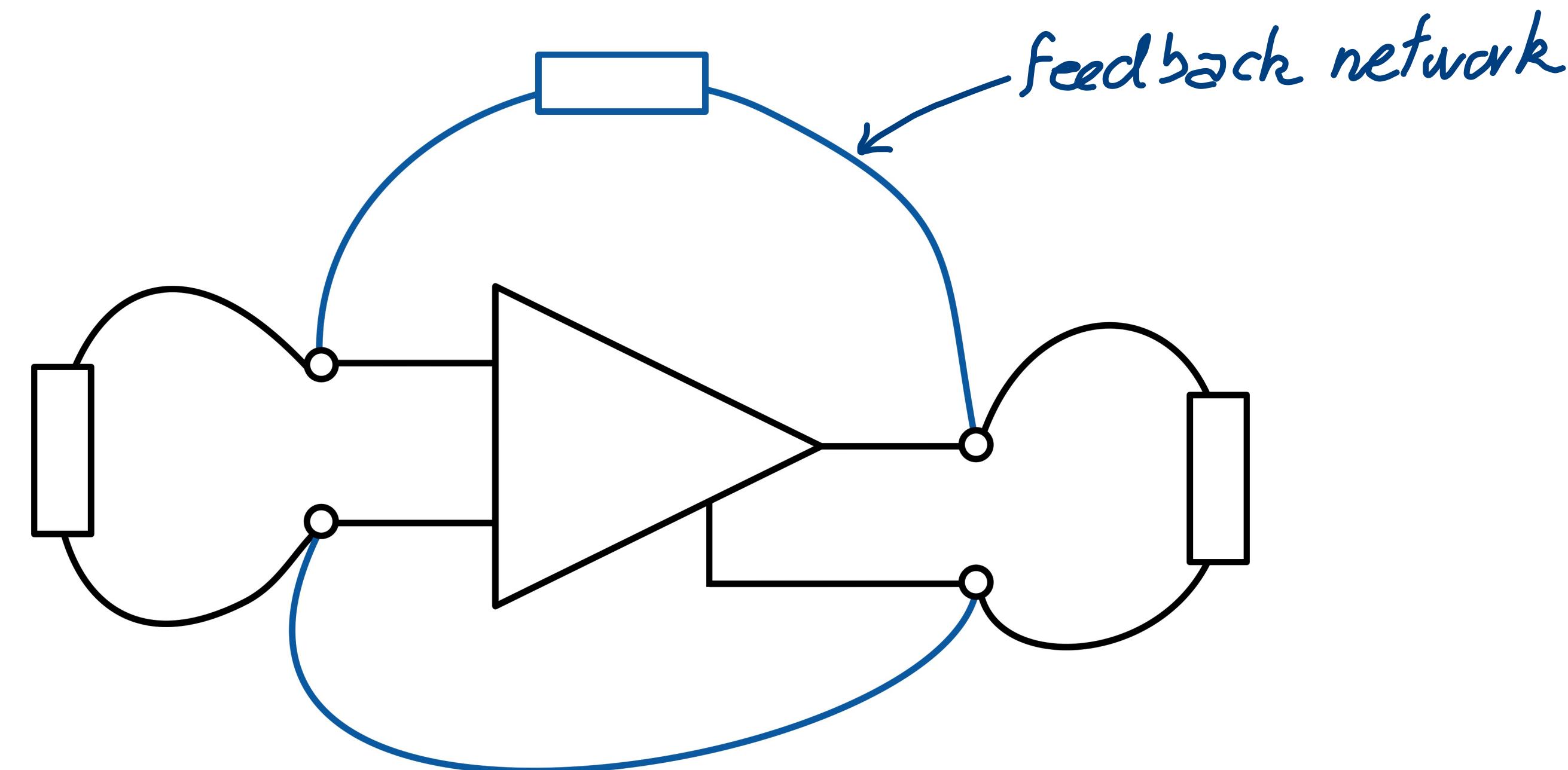5. Circuits with Ideal OA


Nullor circuits are based on **Feedback Networks** coupling the input and output ports



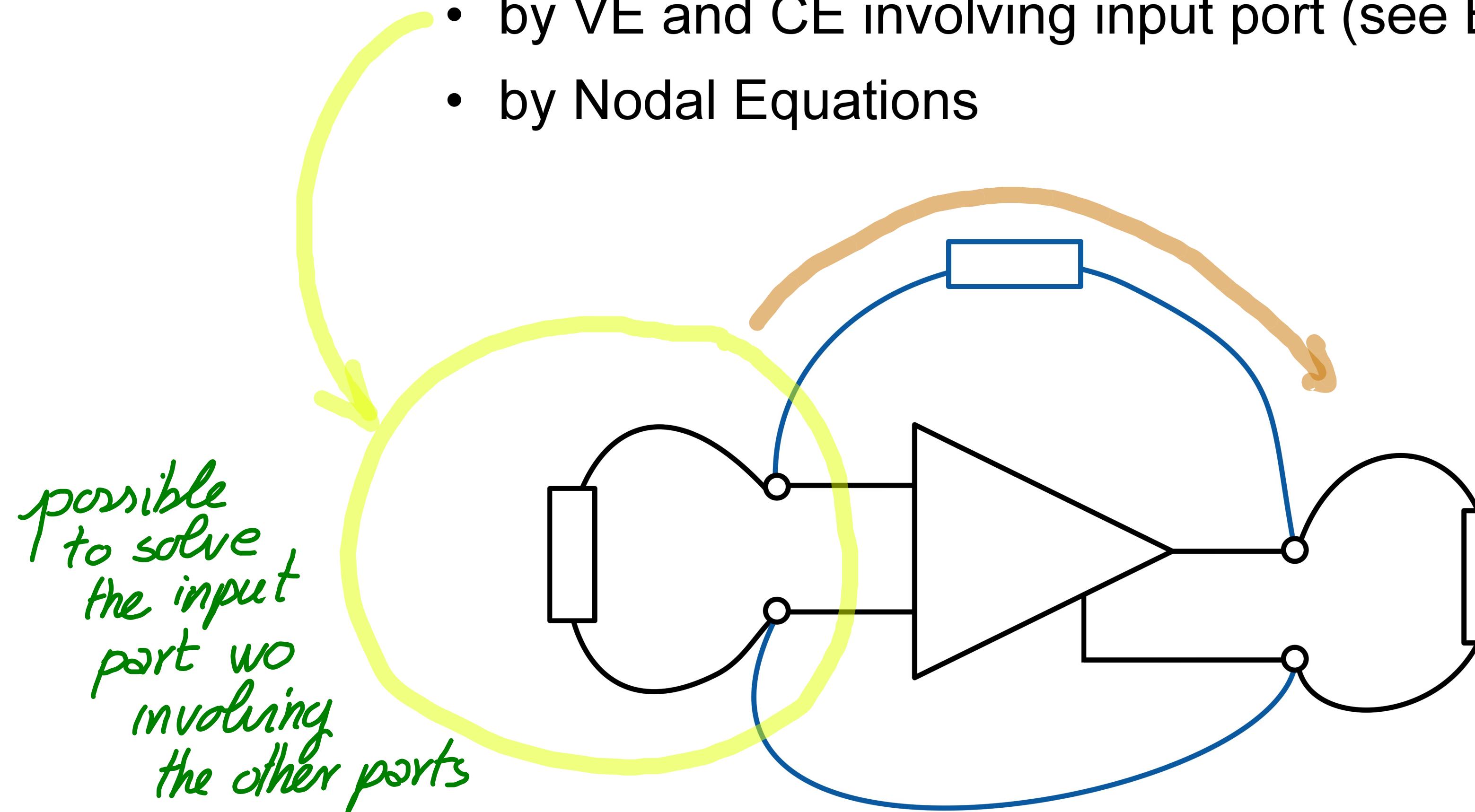5. Circuits with Ideal OA


Analysis:

- by VE and CE involving input port (see Book)
- by Nodal Equations



5. Circuits with Ideal OA


The Inverting OA circuit

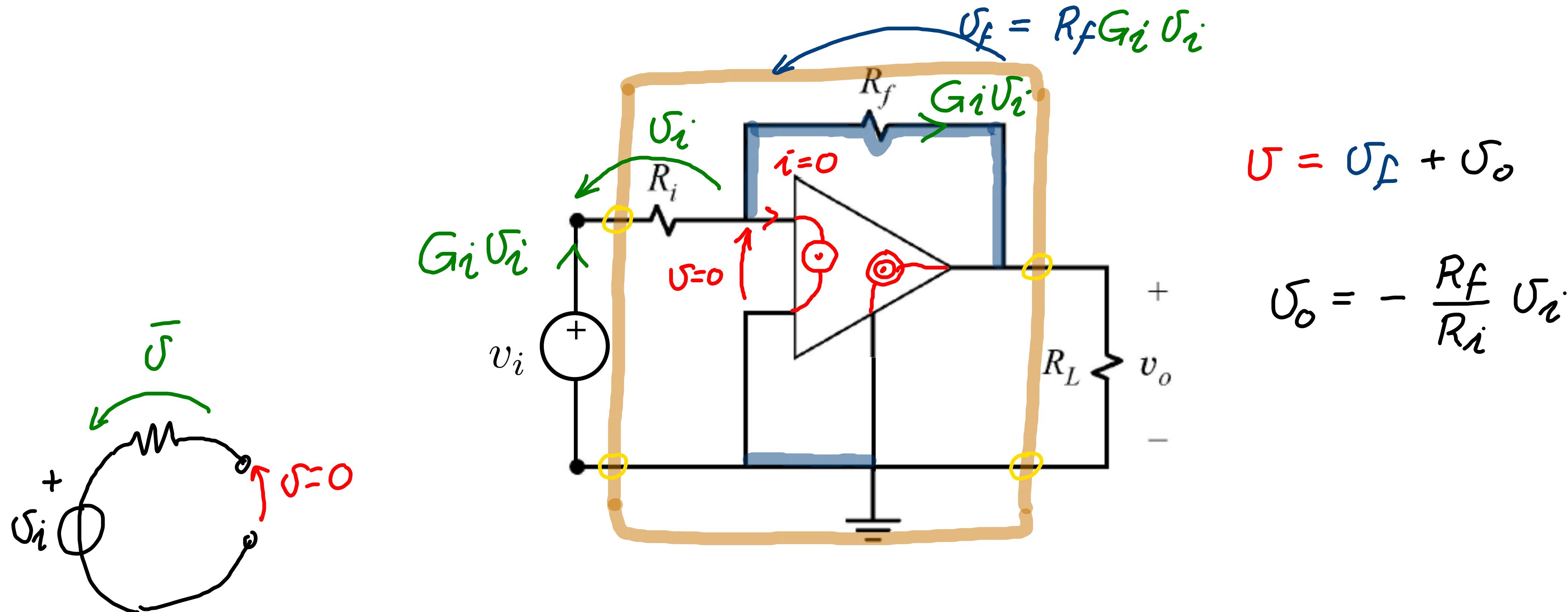

5. Circuits with Ideal OA

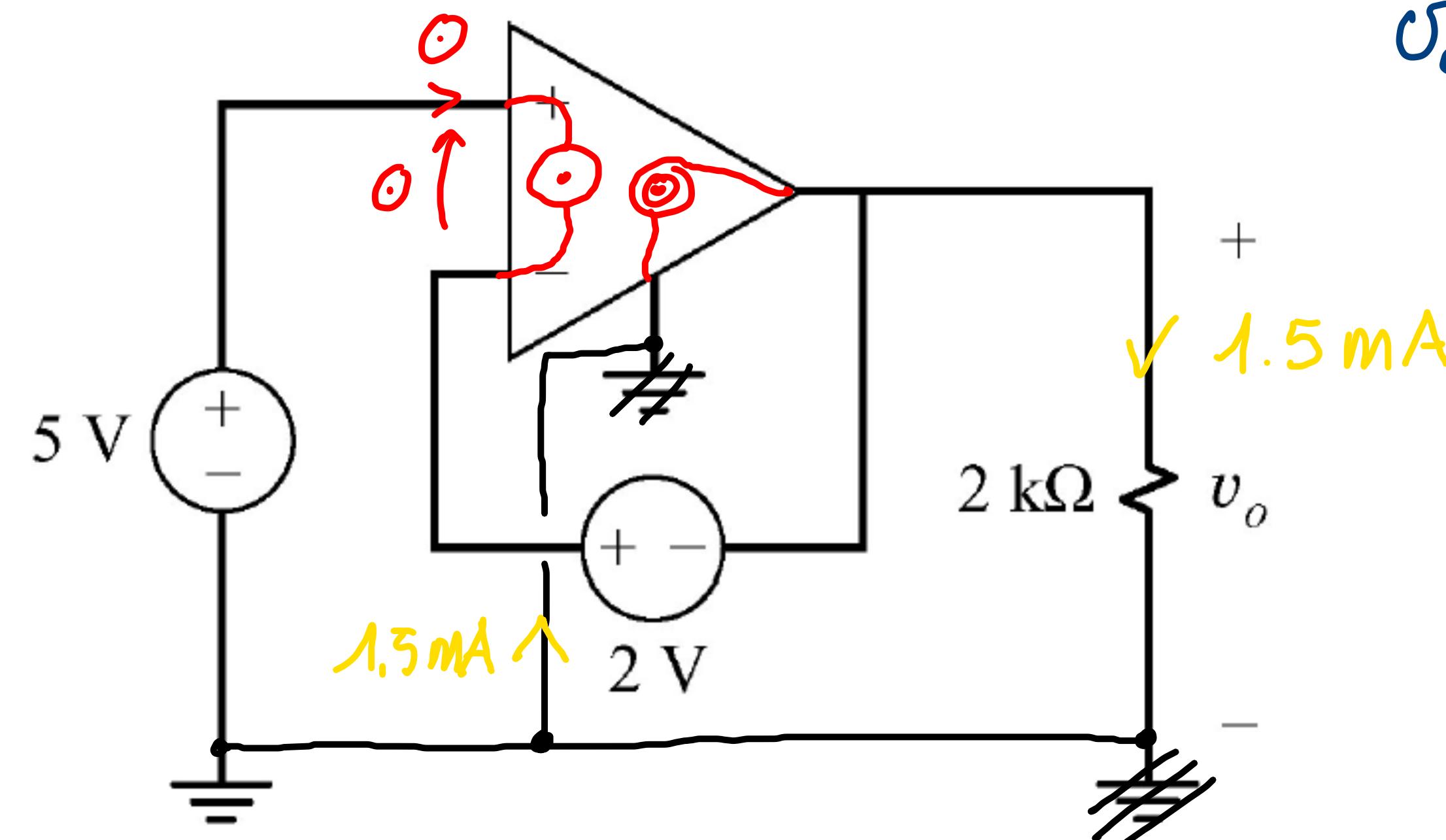Problem: compute v_o

CHAPTER 4 —————
The Operational Amplifier
(Op Amp)



$$5V - 0V - 2V - V_o = 0$$


$$V_o = 3V$$

Figure P4.2-7

Fundamentals of Electric Circuit Analysis, by Clayton Paul

5. Circuits with Ideal OA


The Non Inverting OA circuit

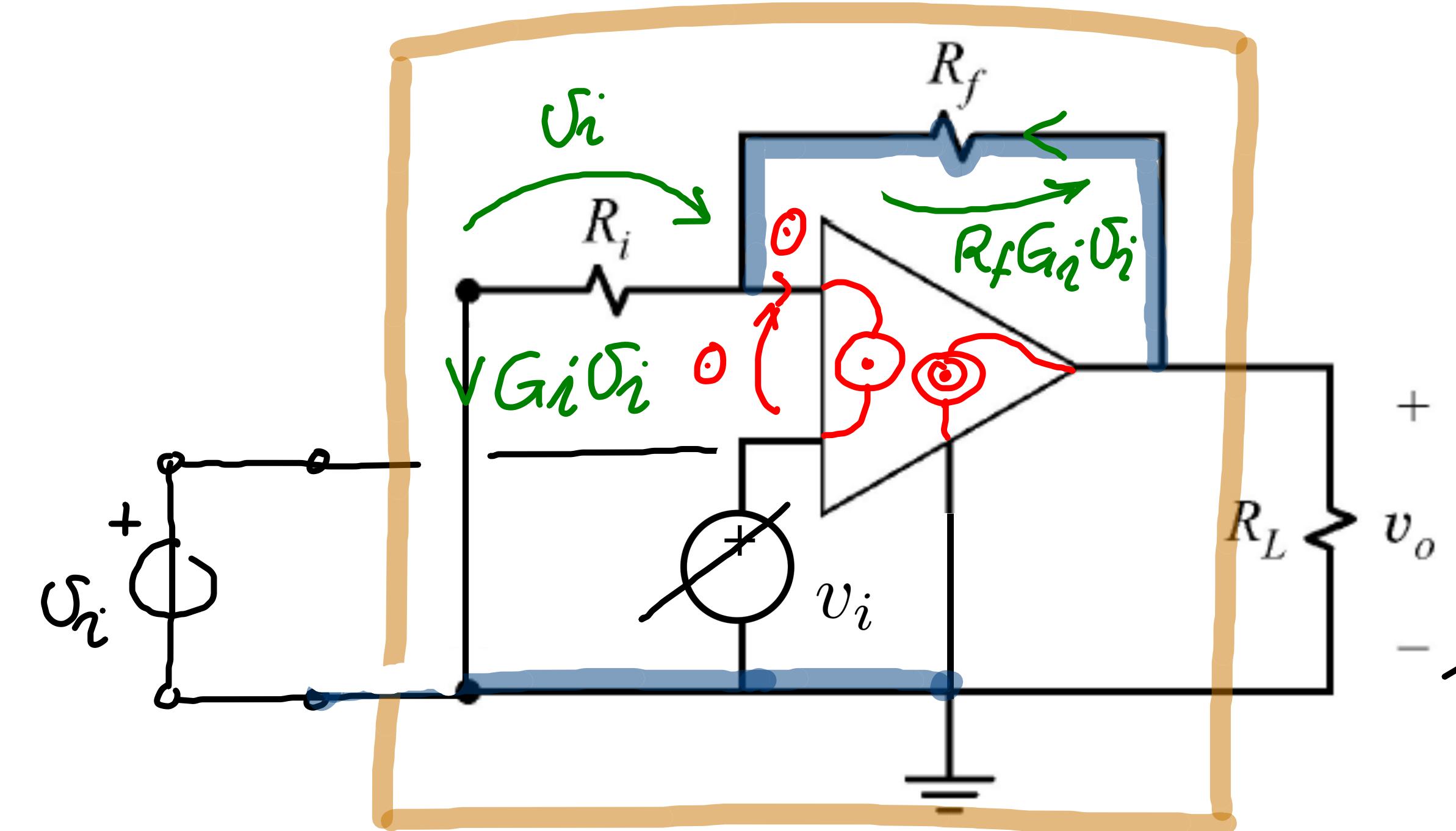



$$\begin{aligned}
 v_o &= R_f G_i v_i + v_i \\
 &= \left(\frac{R_f}{R_i} + 1 \right) v_i
 \end{aligned}$$

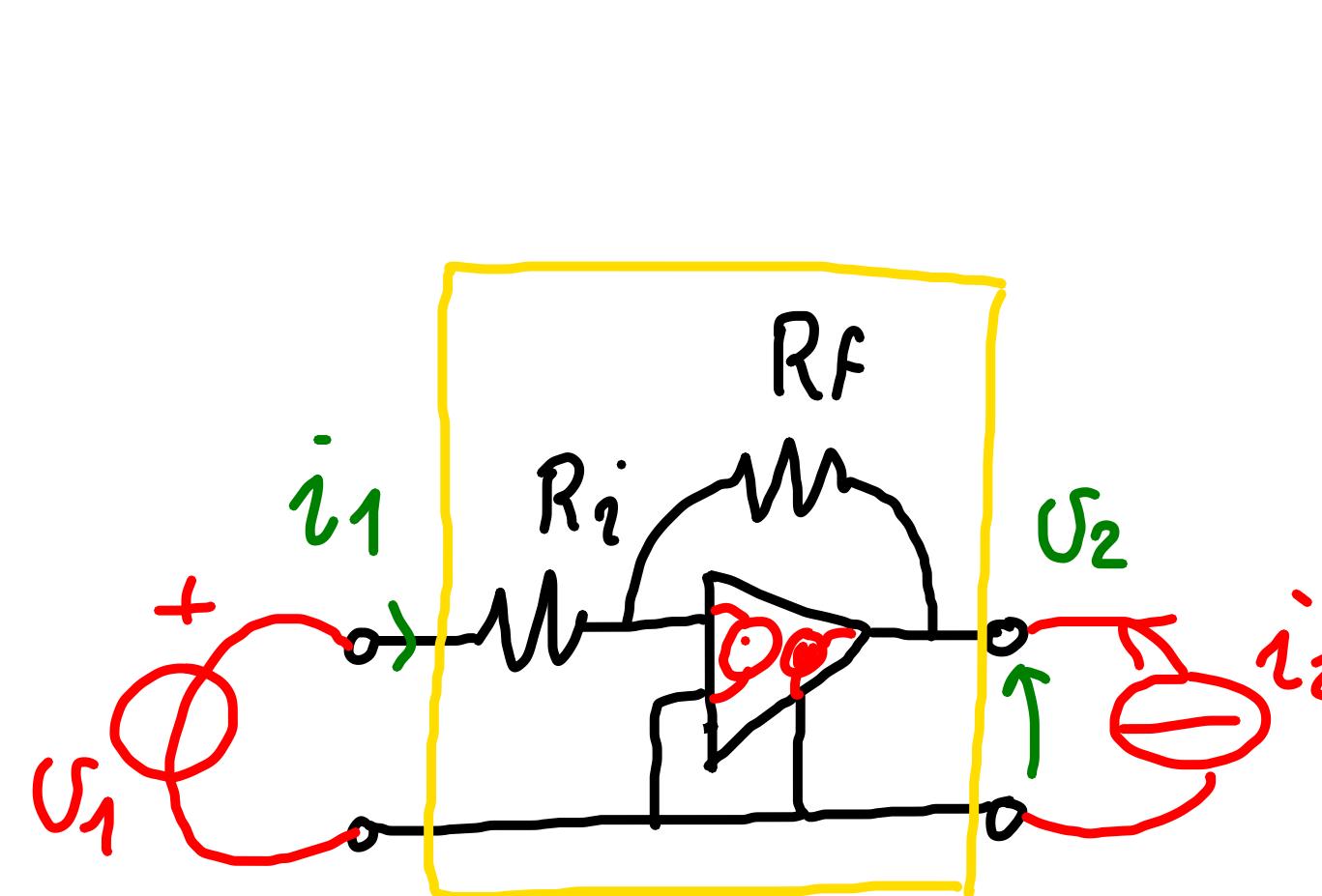5. Circuits with Ideal OA


Hybrid characteristics and eq. circuits for the inverting and non-inverting OA circuits



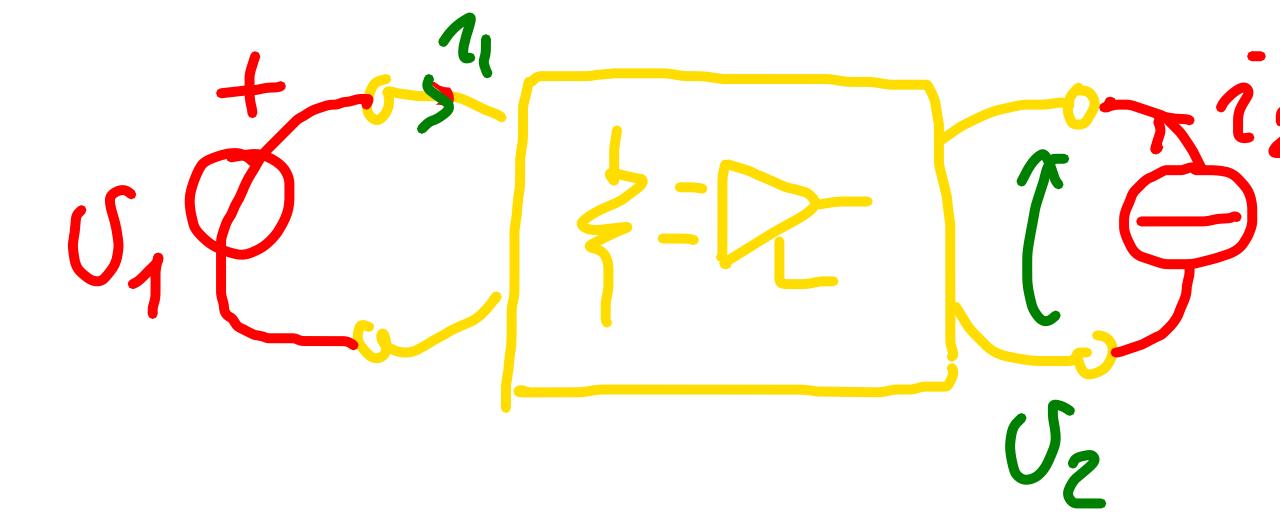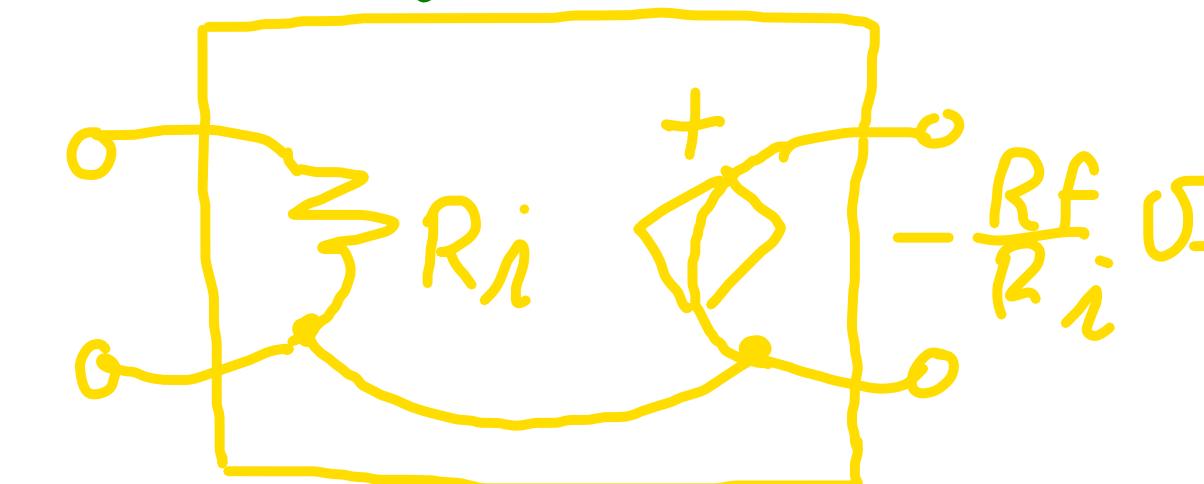
$$\begin{cases} i_1 = G_i U_1 \\ U_2 = -\frac{R_F}{R_i} U_1 \end{cases}$$


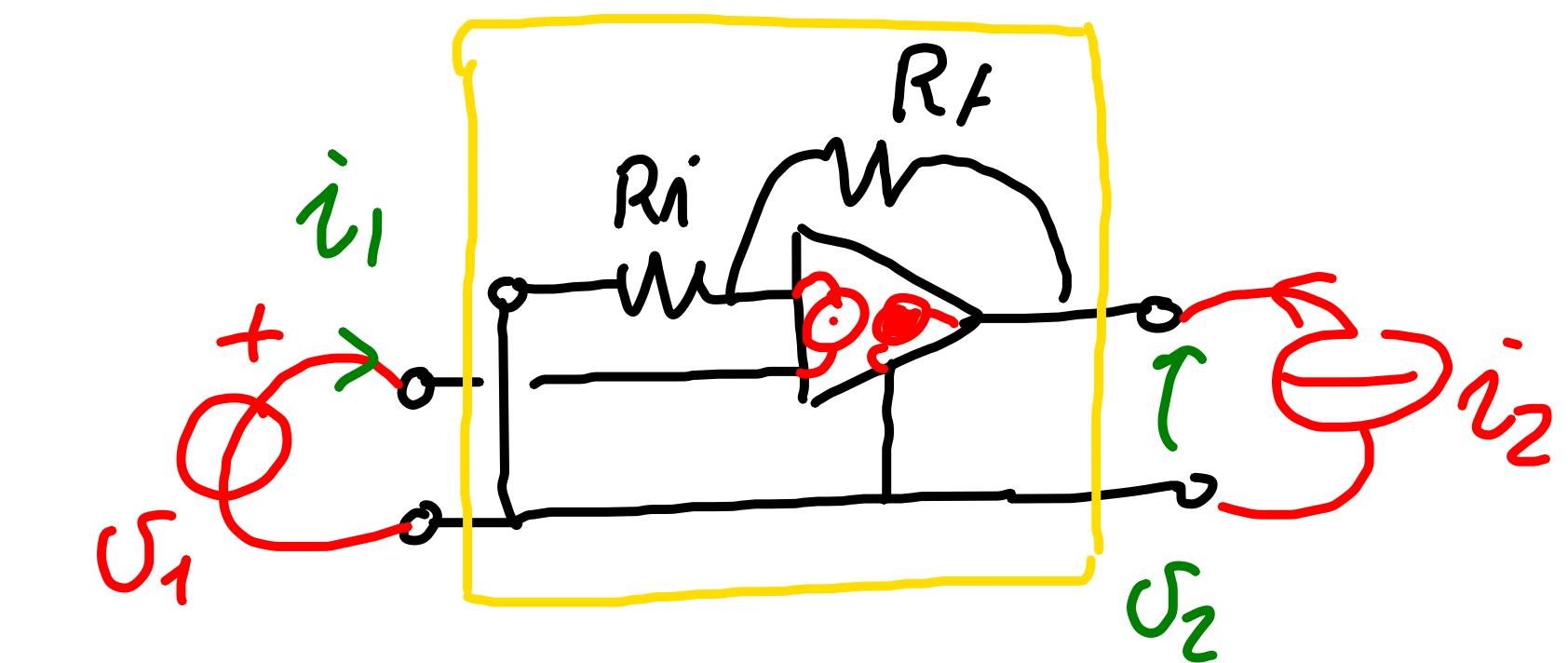
$$\begin{bmatrix} i_1 \\ U_2 \end{bmatrix} = \begin{bmatrix} G_i & 0 \\ -\frac{R_F}{R_i} & 0 \end{bmatrix} \begin{bmatrix} U_1 \\ i_2 \end{bmatrix}$$


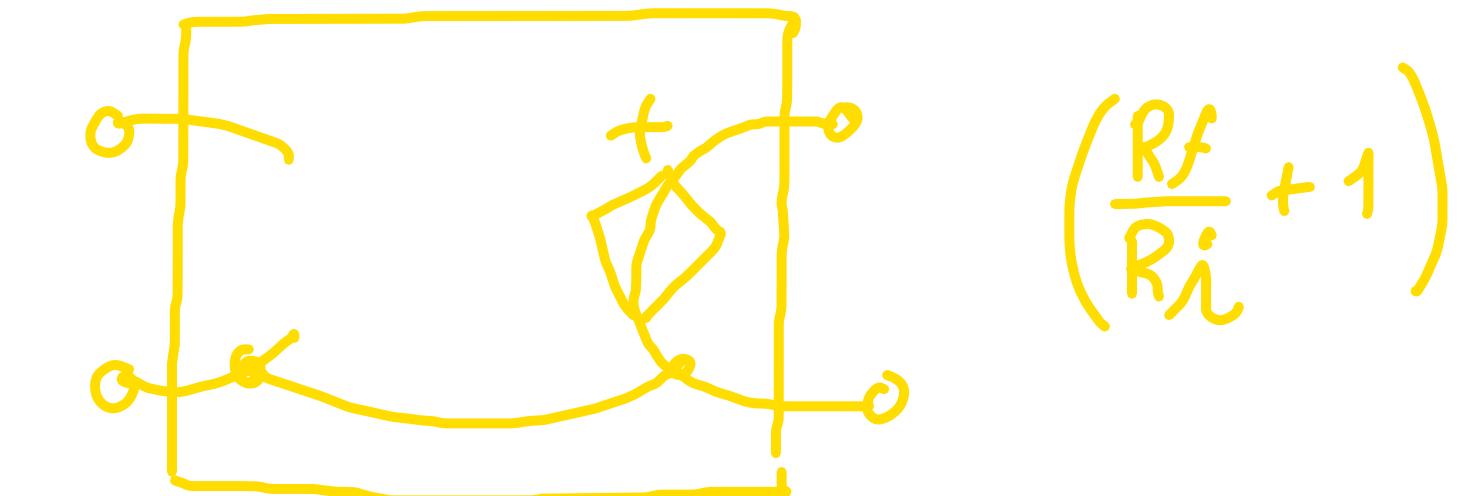
$$\begin{cases} i_1 = 0 \\ U_2 = \left(\frac{R_F}{R_i} + 1 \right) U_1 \end{cases}$$



$$\left(\frac{R_F}{R_i} + 1 \right)$$

5. Circuits with Ideal OA

Example: compute v_o as function of v_i


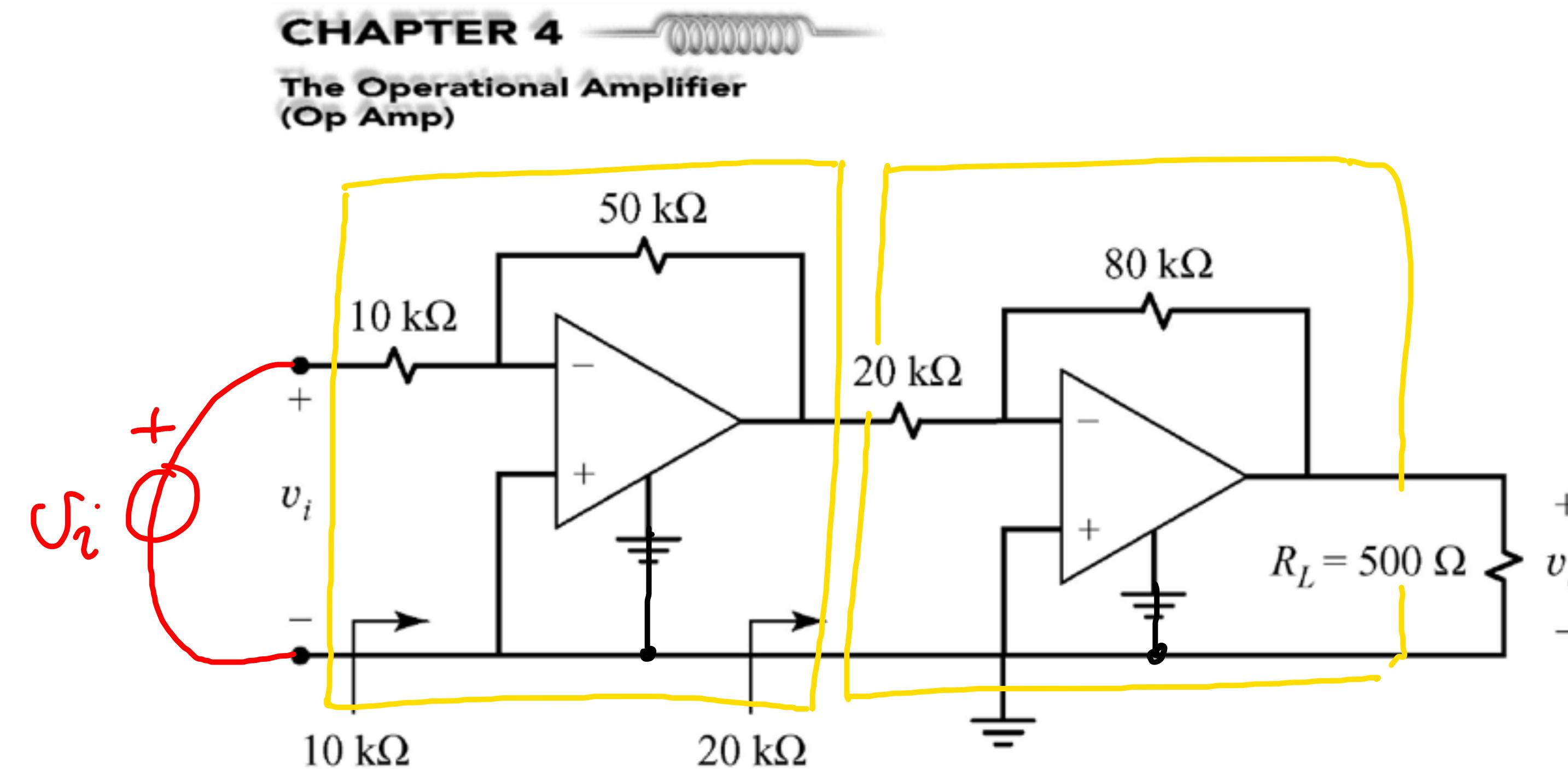
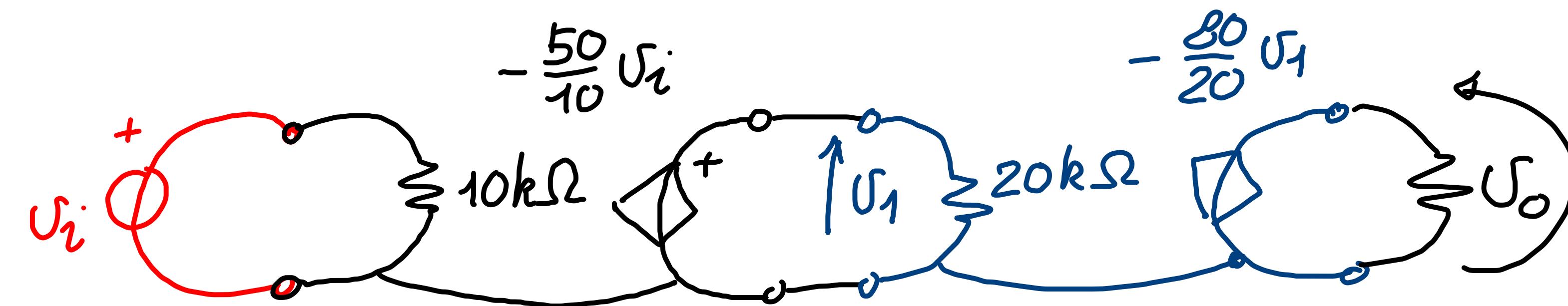


Figure 4.8
Example 4.1.



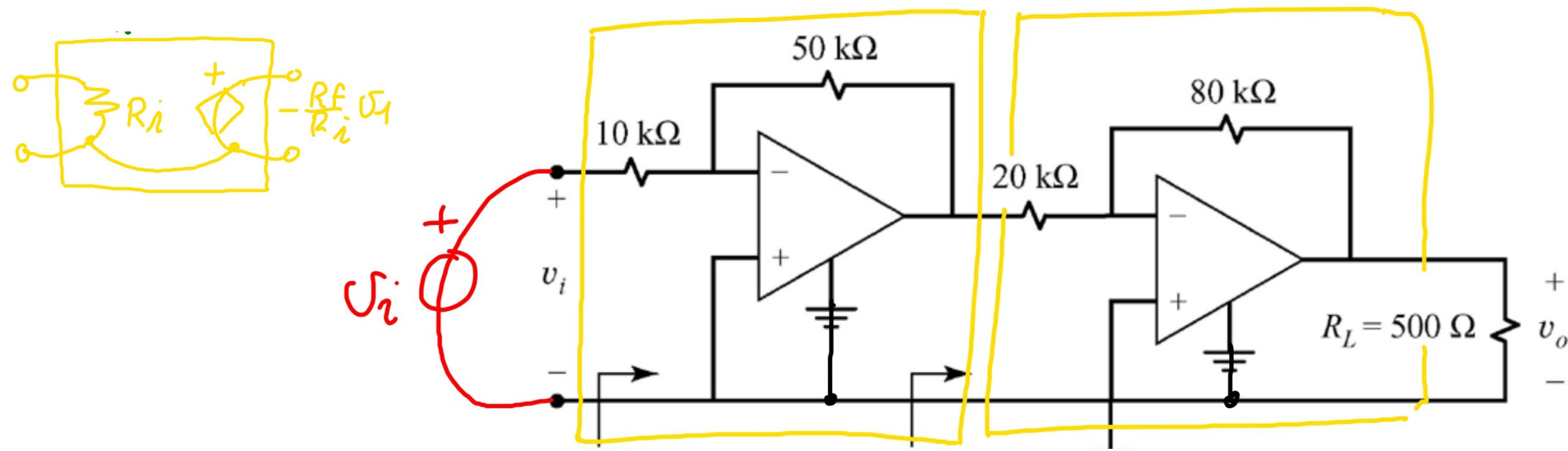
Fundamentals of Electric Circuit Analysis, by Clayton Paul



$$v_o = -4v_1 = -4(-5v_i) = 20v_i$$

5. Circuits with Ideal OA

Example: compute v_o

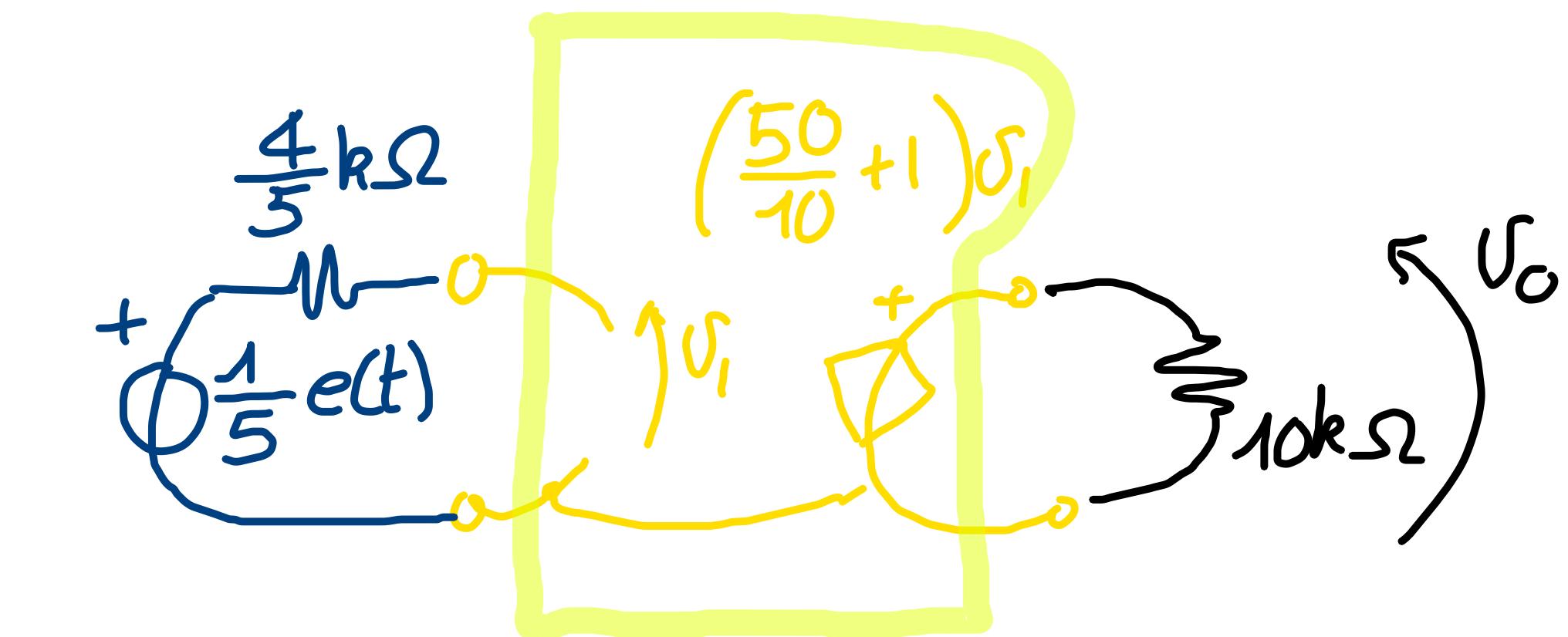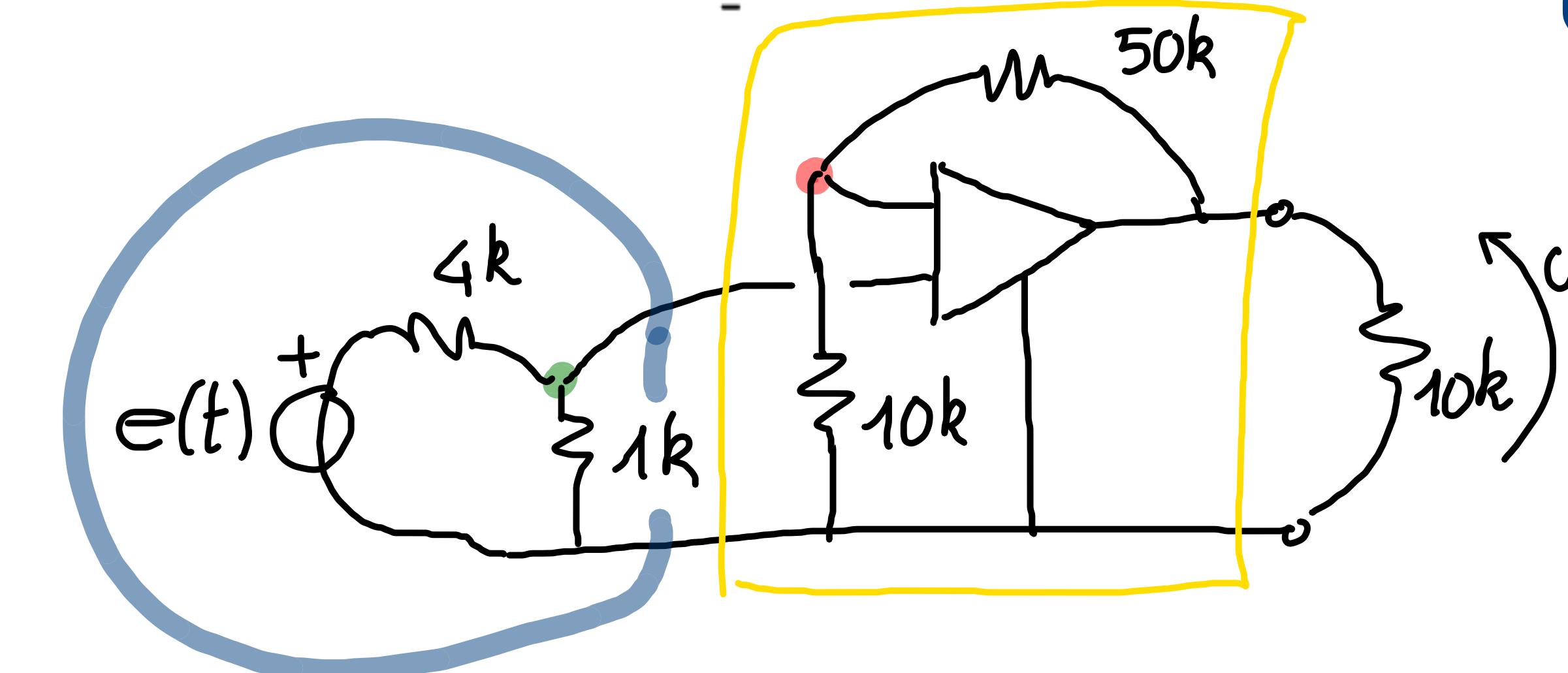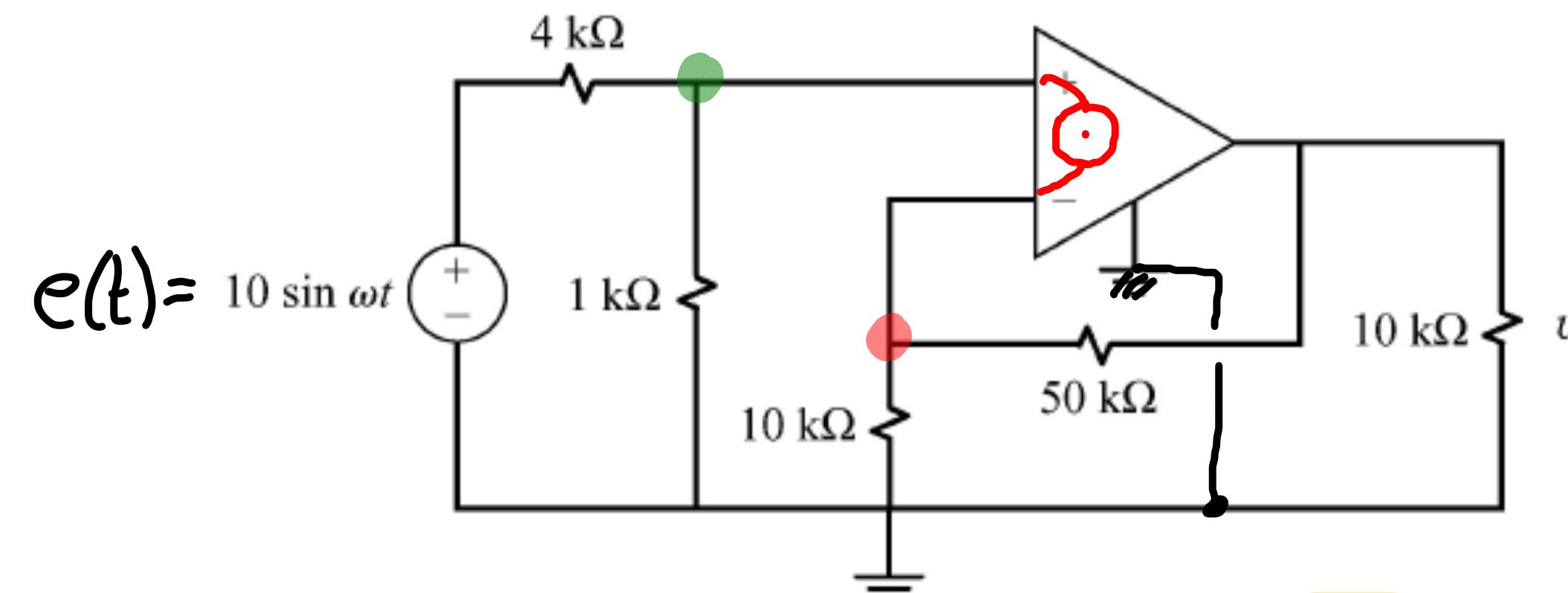

$$v_o = 6v_1 = 6 \frac{1}{5} e(t)$$